

Digital Electronics Circuits

Dr. Eleni Akrida
eleni.akrida@durham.ac.uk



Overview of today's lecture

- Adder
- Subtractor
- Decoder
- Mux
- Tristates
- Simple ALU

Key circuits

Combinatorial/combinational circuits:

(Output depends only on current input)

Adders – add the contents of two registers

Decoders – use a binary number to activate a single line

Multiplexors – use a binary number to select an input

Sequential circuits

(Output depends on state and input, i.e. history of input)

Latches / flip-flops – basic memory element

Half-Adder

Based on 8 simple rules:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \text{ with Carry}$$

XOR

Carry flag

0

0

0

1

AND

$$\text{Carry} + 0 + 0 = 1$$

$$\text{Carry} + 0 + 1 = 0 \text{ with Carry}$$

$$\text{Carry} + 1 + 0 = 0 \text{ with Carry}$$


$$\text{Carry} + 1 + 1 = 1 \text{ with Carry}$$

Inputs: A, B

Outputs: Sum, Carry

A	B	XOR	AND
		Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


10

 

Adder

Input is not just A and B, but A, B and **the carry from the previous bit**

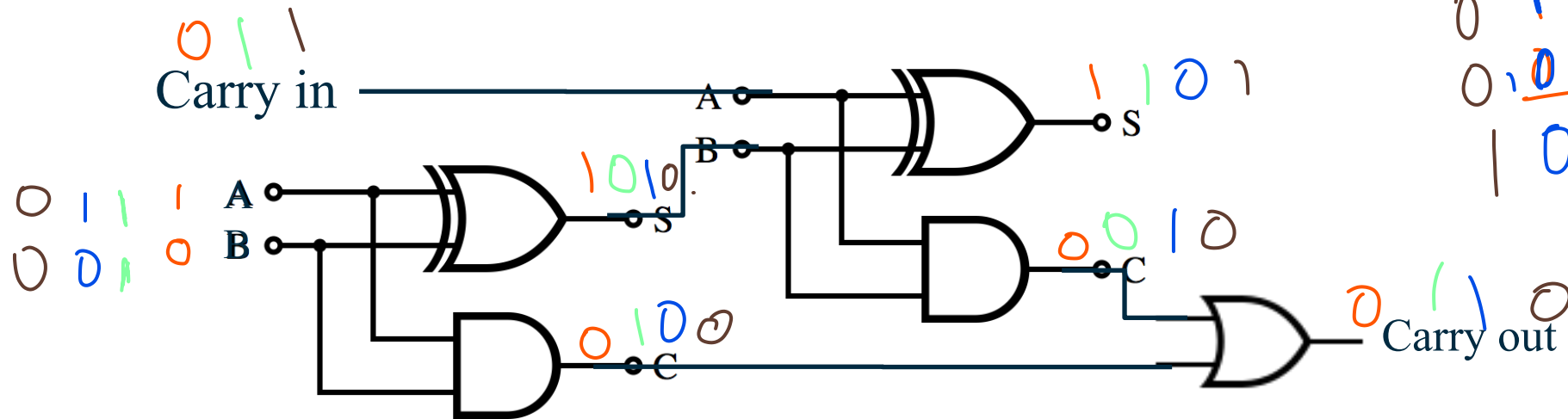
Use two half-adders: Add A and B first, then add in the carried bit:



“Full adder”

Chaining adders

How to add two 4 bit registers:

 


More full-adders can be chained together to give 8-, 16- or 32-bit adders.

Subtractor

Recall that we can create a **twos-complement negative** by inverting each bit and adding 1.

 We subtract b from a by **adding $-b$** .




The NOT gates and setting $C_{in}=1$ give the effect of converting b to $-b$.

Decoder

We have a large bank of memory (say 2^{32} bytes = 4GB).

We want to use 32 bits to address a byte.

 How do we get 32 set bits representing a binary number (address), to activate a given byte from the 4 billion possible?




This is what a decoder does:

N inputs. **2^N** outputs.



Only one output is high at a time.

Which one depends on the input.

 

Decoder

2-bit decoder:

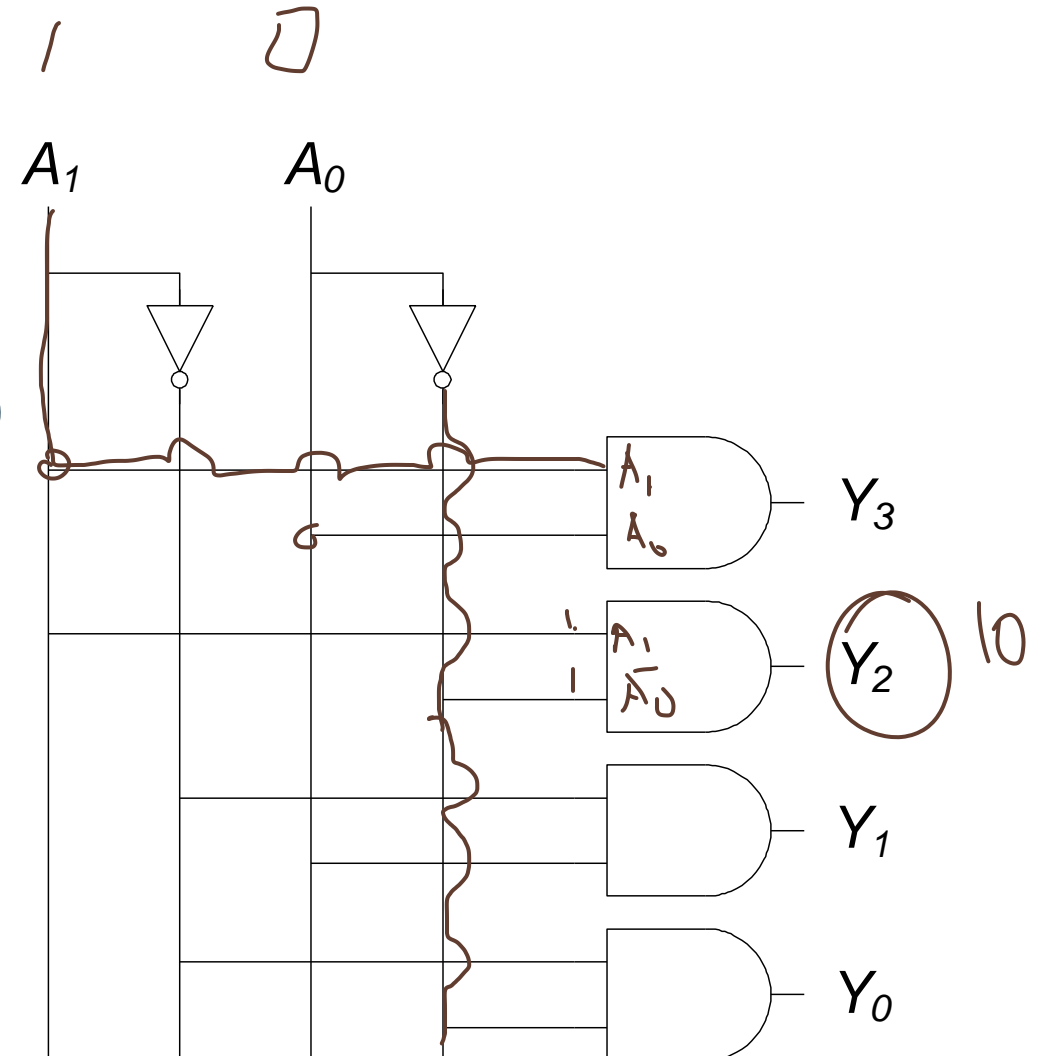 


Decoder


Larger decoders require multi-input AND gates to be constructed in two-level logic.

This requires a lot of circuitry for large decoders.

 
Can create deeper circuits with fewer transistors (i.e. less silicon), at the cost of slower response.



3-bit or '3-8' decoder

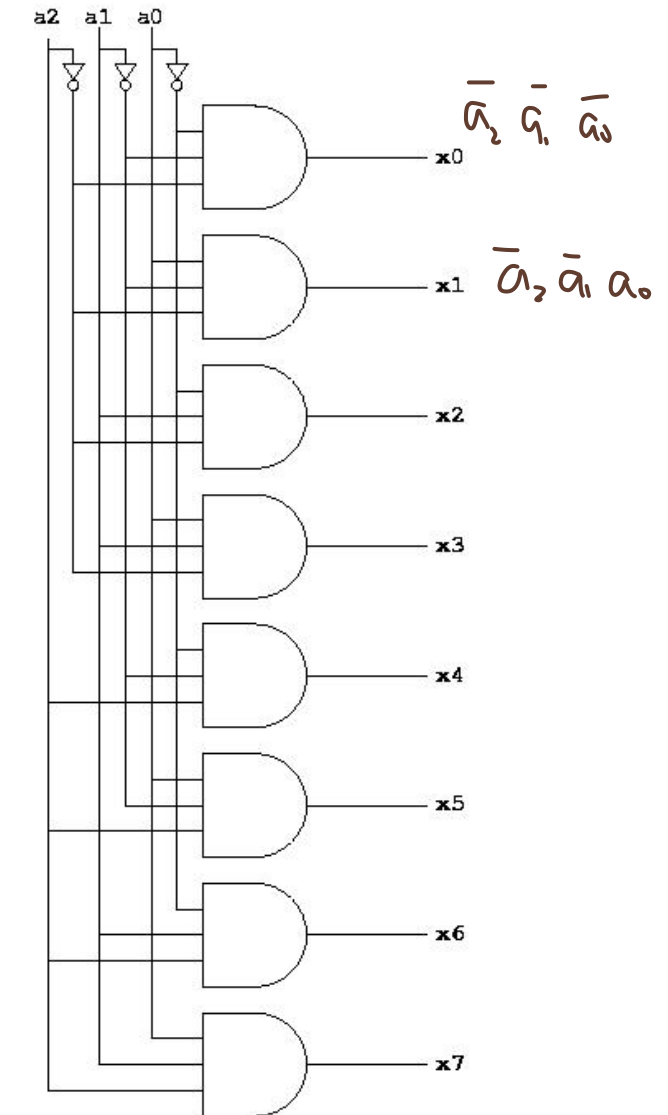

Mux (multiplexor)

 


Compressed version of the truth table

S	D ₁	D ₀	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

S	Y
0	D ₀
1	D ₁

2-to-1 line multiplexor

 


A multiplexor has **$k+2^k$ inputs** and **1 output**.

The first k inputs (selector) represent a binary number.

The output takes the value of the remaining input indexed by this binary number.


Consider many memory locations connected to the inputs. Using the selector we can select which is loaded into a register connected to the output.

Truth tables: Tristate

 


Input	Enable	Output
0	0	Floating
0	1	0
1	0	Floating
1	1	1


Linear truth table

 

 A single transistor could work, but the output is not driven.




Truth tables: Inverting Tristate

 



Input	Enable	Output
0	0	Floating
0	1	1
1	0	Floating
1	1	0

Linear truth table

 

Here the output is driven by direct connection to VDD or ground.


Truth tables: Tristate

  

Input	Enable	Output
0	0	Floating
0	1	0
1	0	Floating
1	1	1

Linear truth table

Mux (multiplexor)

 

S	D ₁	D ₀	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 S &= 1 \\
 Y &= D_0 \bar{S} + D_1 S \\
 Y &= D_0 \cdot 1 + D_1 \cdot 1 \\
 &= D_0 + D_1 \\
 &= D_1
 \end{aligned}$$


A multiplexor has **$k+2^k$ inputs** and **1 output**.

The first k inputs (selector) represent a binary number.

The output takes the value of the remaining input indexed by this binary number.

Consider many memory locations connected to the inputs. Using the selector we can select which is loaded into a register connected to the output.



2-to-1 line multiplexor

 


$$\begin{aligned}
 Y &= D_0 \bar{S} + D_1 S \\
 S &= 0 \quad Y = D_0 \bar{0} + D_1 \cdot 0 \\
 &= D_0 \cdot 1 + 0 \\
 &= D_0
 \end{aligned}$$

Mux


4-to-1 line multiplexor

  

(a)

 

(b)

 

(c)

- a) two-level logic, requiring multiple input gates.
- b) Using tri-state buffers – take value of input if activated, otherwise floating value.
- c) Using hierarchical logic

Building a simple ALU

