

Digital Electronics

Timing and Advanced Adders

Dr. Eleni Akrida
eleni.akrida@durham.ac.uk




Overview of today's lecture

- Timing
- Critical Paths
- Glitches
- Ideas for faster adders

Timing

 In any physical gate or circuit there is a delay between the input changing and the output adjusting appropriately.



Timing


In any physical gate or circuit there is a delay between the input changing and the output adjusting appropriately.

Propagation delay: t_{pd}

the max delay before the output is stable.

Contamination delay: t_{cd}


the min delay before the output changes.

 

Timing

- Delay is caused by
 - Capacitance and resistance in a circuit
 - The speed of light limitation
- Reasons why t_{pd} and t_{cd} may be different:
 - Different rising and falling delays
 - A circuit may have multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold

Critical paths

 


In a circuit the **critical path** is the path determining the propagation delay of the circuit – i.e. the **longest path** in the circuit: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$

The **short path** is the path determining the contamination delay of the circuit – i.e. the **shortest path** in the circuit: $t_{cd} = t_{cd_AND}$

Glitches

 Sometimes the output can **temporarily** move to an incorrect value before stabilising. This is called a **glitch**.



A=0, B=1, C=1

What happens when B falls to 0?


Mux delays

4-line multiplexor circuits.


Different characteristics
for **selector change**
and **data change**

Gate	t_{pd} (ps)
NOT	30
AND	60
3-AND	80
4-OR	90
Tristate (D)	50
Tristate (S)	35

“Canonical” Design:

 

Tristate gates design:

 


Mux delays

4-line multiplexor circuits.

Different characteristics
for **selector change**
and **data change**


Gate	t_{pd} (ps)
NOT	30
AND	60
3-AND	80
4-OR	90
Tristate (D)	50
Tristate (S)	35

Hierarchical Design:

 

Prefer (b) when data
changes last,
but prefer (c) when
control changes last

Tristate gates design:

 


$$\begin{aligned} t_{pd_sy} &= t_{pd_INV} + t_{pd_AND2} + t_{pd_TRI_sy} \\ &= 30 \text{ ps} + 60 \text{ ps} + 35 \text{ ps} \end{aligned}$$

$$(b) \quad = \mathbf{125 \text{ ps}}$$

$$\begin{aligned} t_{pd_dy} &= t_{pd_TRI_ay} \\ &= \mathbf{50 \text{ ps}} \end{aligned}$$

Adder

 The full adder circuit we have looked at takes **3 gate delays** for the carry out to be computed:




If we can **pre-compute the first level**, there are only 2 gate delays once the carry in arrives.

N.B. I am counting all gates as 1 time step. In reality some take longer than others.

Ripple adder

 The computation of the carry bit **ripples** through the chained adders:




A k -bit ripple adder will take $3+2(k-1)=2k+1$ gate delays to compute C_{out} .

So a 32-bit adder takes 65 gate delays!

Faster adders - idea

8-bit ripple adder takes 17 gate delays.

 

Time 9: Answer if $C_4=0$ and if $C_4=1$

Time 9: Answer and C_4

Time 11: Correct Answer

Key idea: for later bits pre-compute the outcome with both carry in and no carry in, then quickly select the right answer.

Faster addition at the expense of more circuitry.

Carry-Lookahead Adder

The 8 rules of binary addition:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \text{ with } C_{out}$$

$$C_{in} + 0 + 0 = 1$$

$$C_{in} + 0 + 1 = 0 \text{ with } C_{out}$$

$$C_{in} + 1 + 0 = 0 \text{ with } C_{out}$$

$$C_{in} + 1 + 1 = 1 \text{ with } C_{out}$$

Define two functions.

Generate: $G(A,B) = 1$ if A and B would cause C_{out} even if $C_{in} = 0$.


Propagate: $P(A,B) = 1$ if A and B would cause C_{out} if $C_{in} = 1$.

$$G(A,B) = A \text{ AND } B$$

$$P(A,B) = A \text{ OR } B$$


Carry occurs if it is **generated** or if there is carry in and it is **propagated**: $C_{out} = G(A,B) + P(A,B) \cdot C_{in}$

Carry-Lookahead Adder

 

$$\begin{aligned}C_{out} &= G_4 + P_4 \cdot C_3 \\&= G_4 + P_4 \cdot (G_3 + P_3 \cdot C_2) \\&= G_4 + P_4 \cdot (G_3 + P_3 \cdot (G_2 + P_2 \cdot C_1)) \\&= G_4 + P_4 \cdot (G_3 + P_3 \cdot (G_2 + P_2 \cdot (G_1 + P_1 \cdot C_{in}))) \\&= G_4 + P_4 G_3 + P_4 P_3 G_2 + P_4 P_3 P_2 G_1 + P_4 P_3 P_2 P_1 \cdot C_{in}\end{aligned}$$

Carry-Lookahead Adder

 


$$C_{out} = G_4 + P_4 G_3 + P_4 P_3 G_2 + P_4 P_3 P_2 G_1 + P_4 P_3 P_2 P_1 \cdot C_{in}$$

We can compute every P_i and G_i in one gate delay


So we can compute C_{out} (and all the intermediate carries) in 3 gate delays (1 for P_i, G_i , an AND layer and an OR layer).

We could compute the full sum in 4 gate delays!

Carry-Lookahead Adder

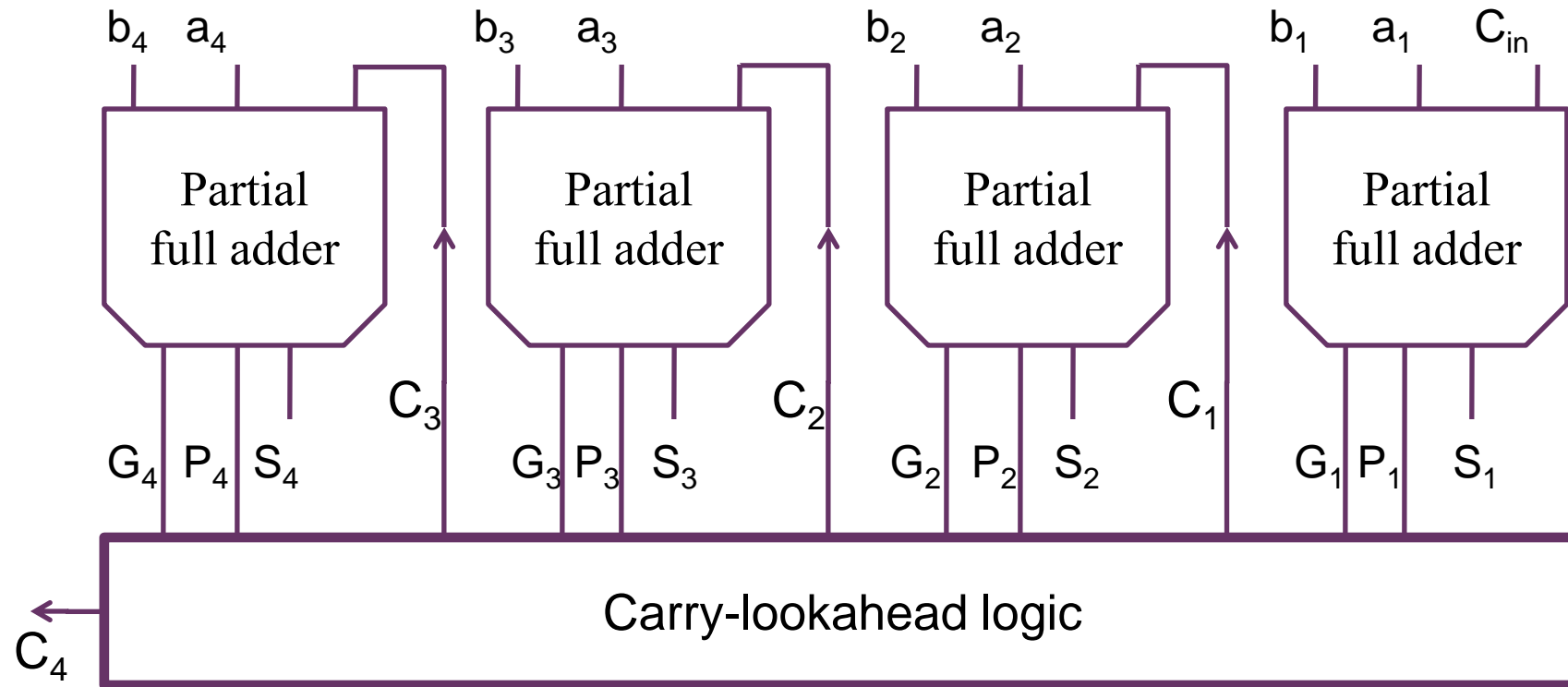


Partial full Adder

 


MSI chip 74x283

- 4-bit CLA adder

 

 
- Notes:**
- Gate depth 4
- Requires gates with many inputs



Carry-Lookahead Adder

We could create a CLA which adds n -bit numbers in constant gate delay.
It would require order n^2 gates and gates taking order n inputs.
This is impractical for large n .


First solution: chain 4-bit CLAs

 

The carry now ripples along the chain 4-times as fast as originally

2-level Carry-Lookahead Adder

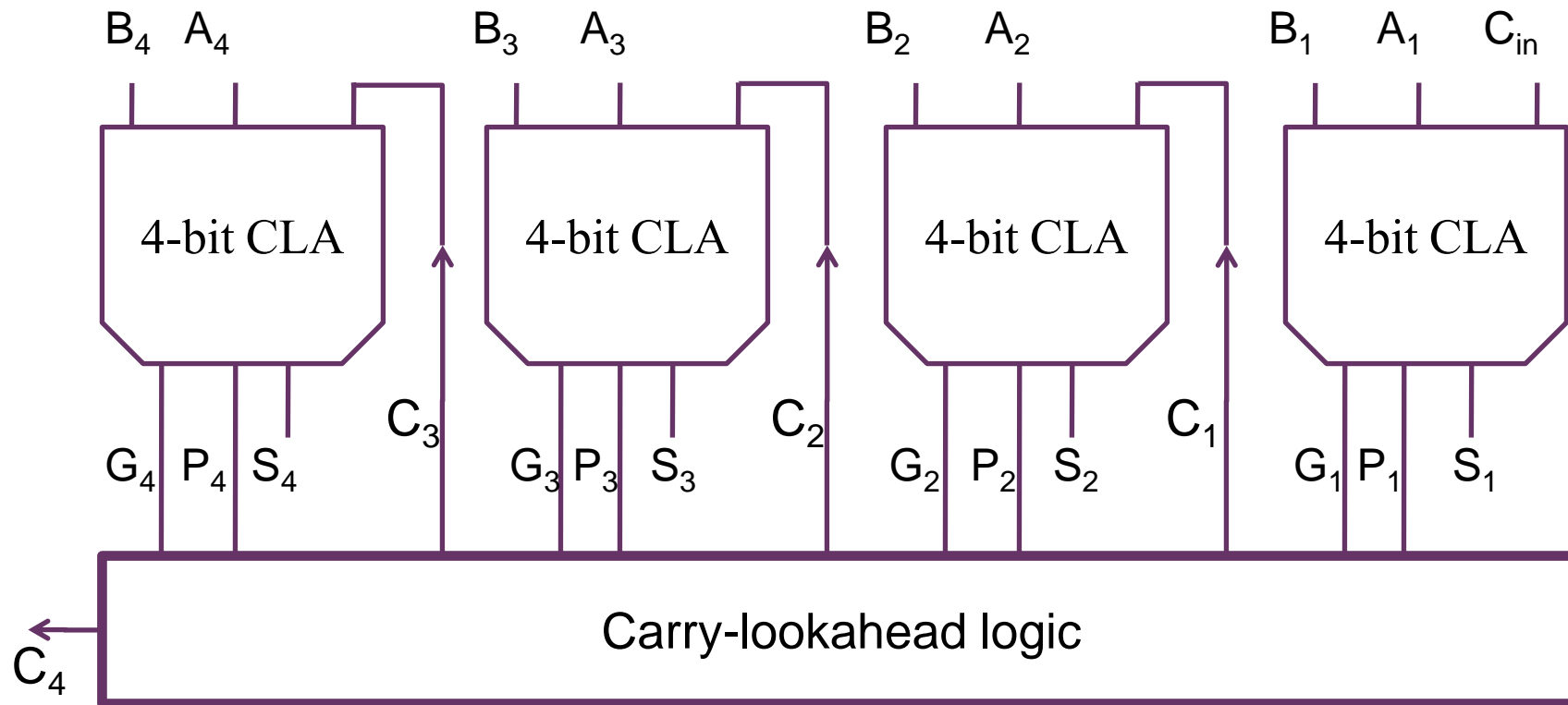Rather than letting the carry ripple through the CLAs, we can pre-compute whether it would be generated or propagated by each CLA.



A_i, B_i, S_i each represent 4 bits.

2-level Carry-Lookahead Adder

We now have a 16-bit 2-level CLA.

Gate delays:

- 1 gate delay to compute first (bit) level G_s , P_s
- 2 gate delays to compute second (block) level G_s , P_s
- 2 gate delays to compute carries across the whole system
- 1 gate delay to compute sums across the whole system

Total **6 gate delays**.

A standard 16-bit ripple carry adder would take 33 gate delays.

These 16-bit adders could be chained to give an n -bit adder with gate delay $2(n/16)+4$.

Alternatively, a 3 (or more) level CLA could be used to create an n -bit adder with delay $O(\log n)$ and not too much circuitry.