

Digital Electronics

Logic Gates and Transistors

Dr. Eleni Akrida
eleni.akrida@durham.ac.uk



Overview of today's lecture

- Transistors
- Logic gates and truth tables
- Logic Levels
- Moore's Law

Transistors

Babbage's Analytical Engine – gears

Early electrical computers – relays or vacuum tubes

Modern computers – **transistors!**

Electrically controlled switches that turn ON or OFF when voltage or current is applied to a control terminal.


Most common transistor is the MOSFET:

Metal-Oxide-Semiconductor Field Effect Transistor.

- 1 billion MOSFETs onto a 1cm^2 chip of silicon.
- Building blocks of almost all digital systems.


Transistors

 - 2 ports (**d** and **s**) are connected depending on voltage of 3rd (**g**)



Transistors

 
- **MOS** transistors are built from semiconductor material, usually silicon.
- **Silicon** is a poor conductor of electricity: all the available electrons (4) are used to form bonds with neighbouring atoms.
- Impurities (**dopants**) provide extra electrons or electron-holes which increase conductivity.




Transistors

The junction between p-type and n-type silicon is **a diode**.

 Current can only flow from p-type to n-type.



anode cathode

 


Transistors

A **capacitor** is two pieces of conductive material separated by an insulator.


If a positive voltage is applied to one side, it accumulates charge Q and the other side accumulates the opposite charge $-Q$.

 It takes time and energy to charge or discharge a capacitor.




Transistors

- nMOS transistor:

 

(a)

 


(b)

When the **gate g** is at 0V, the **diode effect** between n-type and p-type silicon prevents current flowing from **source** to **drain**.

Transistors

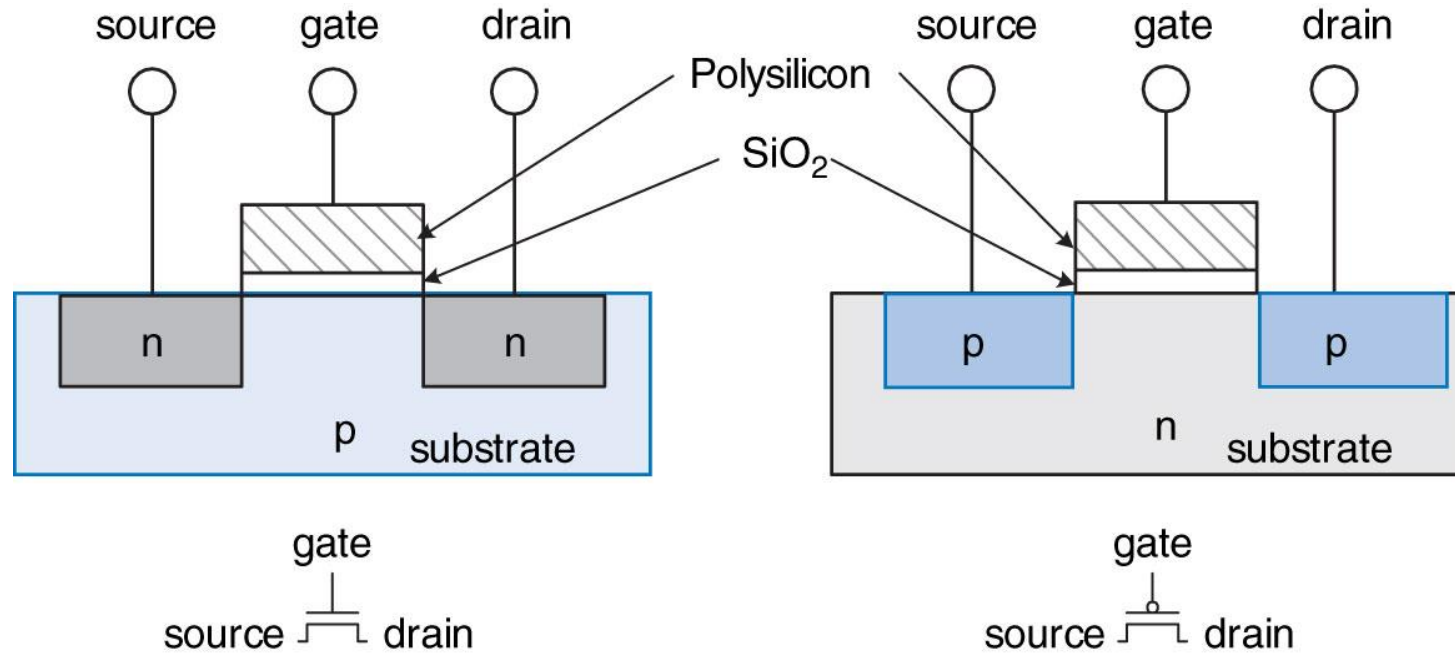- A pMOS transistor is the opposite: **on at g low** and **off at g high**.



(a) nMOS

(b) pMOS

Adding in binary

			1	11	111	111
11100	11100	11100	11100	11100	11100	11100
<u>+01110</u>	<u>+01110</u>	<u>+01110</u>	<u>+01110</u>	<u>+01110</u>	<u>+ 01110</u>	<u>+ 01110</u>
	0	10	010	1010	01010	101010

Based on 8 simple rules:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \text{ with Carry}$$

$$\text{Carry} + 0 + 0 = 1$$



$$\text{Carry} + 0 + 1 = 0 \text{ with Carry}$$

$$\text{Carry} + 1 + 0 = 0 \text{ with Carry}$$

$$\text{Carry} + 1 + 1 = 1 \text{ with Carry}$$

How is this achieved?

  - Using **gates** implementing **Boolean algebra**.
- **Boolean algebra:**
an algebra of two values: **1,0**
or **True/False** or **high/low voltage**.
- Basic operations: AND, OR, NOT
 - $0 \text{ AND } 0 = 0$
 - $0 \text{ AND } 1 = 0$
 - $1 \text{ AND } 0 = 0$
 - $1 \text{ AND } 1 = 1$



Truth tables: AND

- **AND** gate:  Algebraic expression: $Y = A \cdot B$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Linear truth table

AND	0 ^B	1
0 ^A	0	0
1	0	1

Rectangular/Coordinate table

Truth tables: OR

- **OR** gate:  Algebraic expression: $Y = A + B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Linear truth table

OR	0 ^B	1
0 ^A	0	1
1	1	1

Rectangular/Coordinate table

Truth tables: Exclusive OR (XOR)

- XOR** gate:  Algebraic expression: $Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Linear truth table

AND		B	
		0	1
A	0	0	1
	1	1	0

Rectangular/Coordinate table

Truth tables: NOT

- NOT** gate:  Algebraic expression: $Y = \bar{A}$

A	Y
0	1
1	0

Linear truth table


Truth tables: NOR

- **NOR** gate (inverse of OR)



Algebraic expression: $Y = \overline{A + B}$


||

 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Linear truth table

From transistors to gates

- A **NOT** gate: 
- If **A** is **high** then the p-MOS P1 is off and the n-MOS N1 is on, so **Y** is connected to GND, i.e. **low**.
- If **A** is **low** then the p-MOS P1 is on and the n-MOS N1 is off, so **Y** is connected to V_{DD} , i.e. **high**.


A	P1	N1	Y
0	on	off	1
1	off	on	0

 

From transistors to gates

- A **NAND** gate: 

A	B	P1	P2	N1	N2	Y
0	0					
0	1					
1	0					
1	1					

 


Note: 3-wire junctions are connected, but 4-wire junctions are only connected if there is a dot.

From transistors to gates

- A **NAND** gate: 


A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1					
1	0					
1	1					

 

From transistors to gates

- A **NAND** gate: 


A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0					
1	1					

 

From transistors to gates

- A **NAND** gate: 


A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1					

 

From transistors to gates

- A **NAND** gate: 


A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

 

From transistors to gates

- An **AND** gate: 

 Essentially made by combining a NAND and a NOT gate.





Beneath the digital abstraction

A chip does not really deal in 0s and 1s.

The **voltages** are real numbers between 0V and 5V (typically).

We can take 0V to indicate output 0 and 5V to indicate output 1, but we need to tolerate **noise**.

  If the output is 4.9V that is probably meant to be a 1.
But what about 4.1V or 3V or 2.5V?



Supply voltage


The **low** voltage in the system (connected to **ground** or GND) is 0V.

Historically the circuit was powered by connecting to a 5V supply, and the **high** voltage is therefore 5V, called V_{DD} if unspecified.

More modern chips, using much smaller transistors, have moved to $V_{DD} = 3.3V, 2.5V, 1.8V, 1.5V$ and $1.2V$, both to save power and avoid overloading transistors.

The mapping of the continuous voltage measured at any point in the circuit to the discrete 0 and 1 of the digital abstraction is governed by defining **logic levels**.

Logic levels

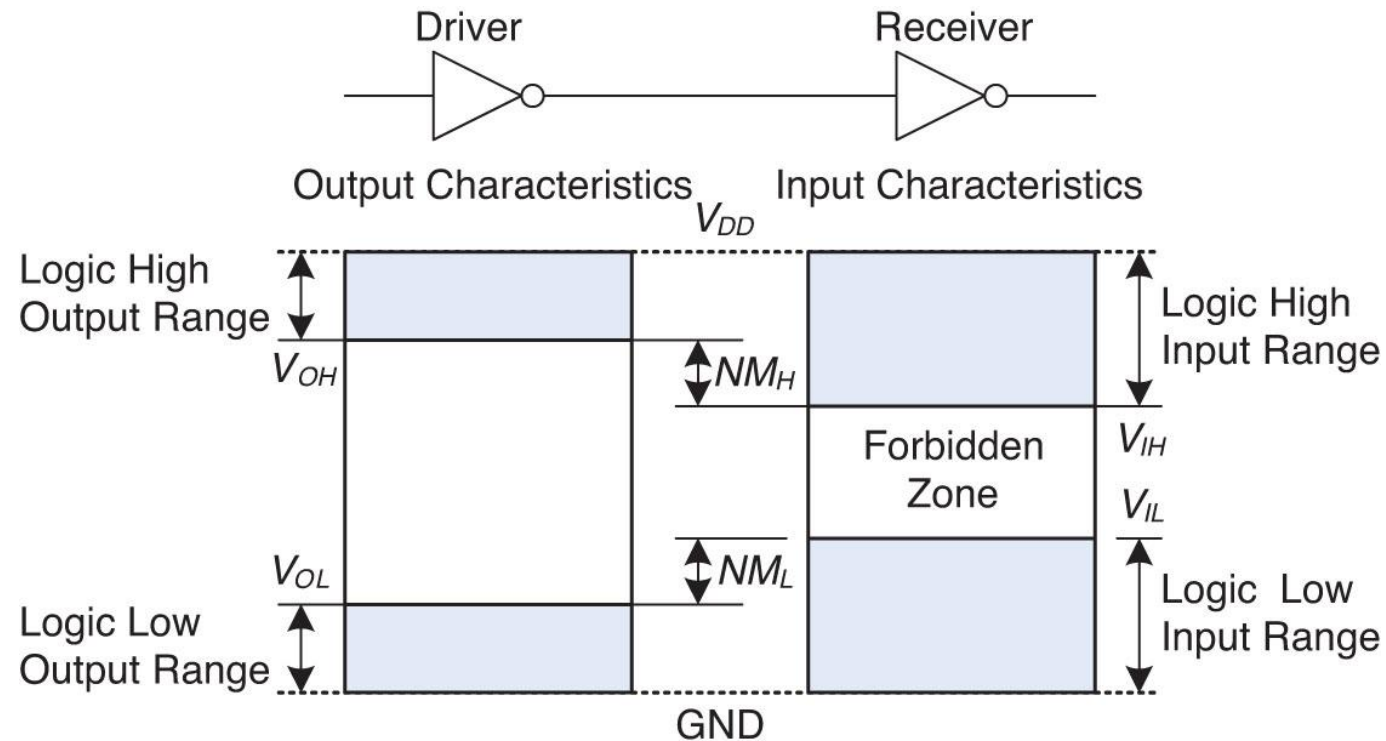

Permitted range for high output: V_{OH} to V_{DD}

Permitted range for low output: GND to V_{OL}

Acceptable range for high input: V_{IH} to V_{DD}

Acceptable range for low input: GND to V_{IL}

Noise margins:

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

The Static Discipline

- The design restriction that you will **only allow circuit elements that all satisfy the same logic levels.**
- This means that (given noise limits) you can successfully apply the **digital abstraction** and **combine elements** without further concern about logic levels or analogue values.
- It does reduce your freedom to include arbitrary elements but makes design much simpler.

Logic Family	V_{DD}	V_{IL}	V_{IH}	V_{OL}	V_{OH}
TTL	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5 - 6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7

Moore's law

Gordon Moore co-founded Intel in 1968.

In 1965 he observed that the number of transistors on a computer chip doubles every year.


Moore's law: normally quoted as “transistor density doubles in 2 years”, or “computer processing power doubles every 18 months”.

Moore's law

Mastering Moore's Law

Intel's progress in packing more transistors on mainstream microprocessor chips


Logarithmic scale

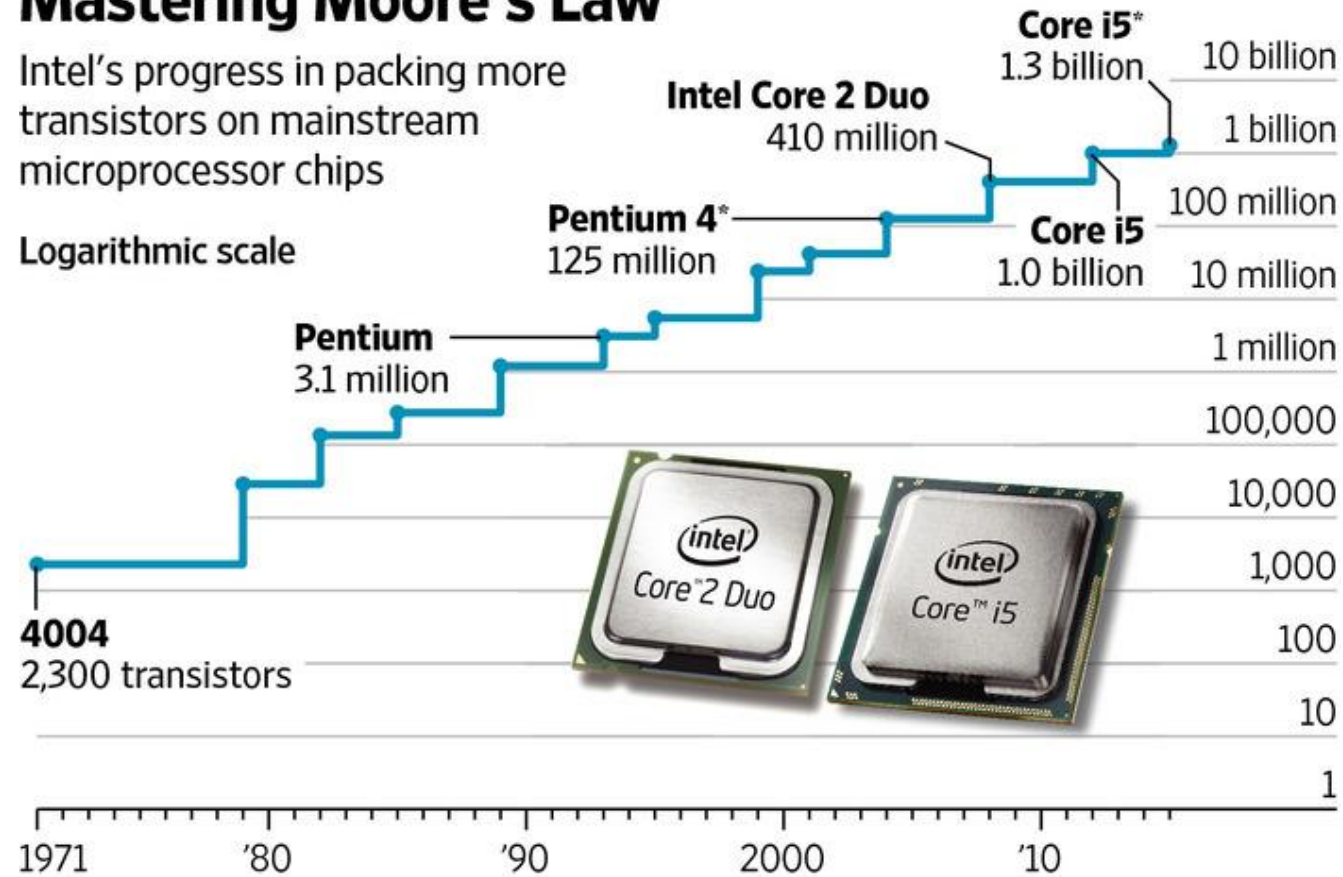

*Upgraded versions of prior models
Source: Intel

THE WALL STREET JOURNAL.

Moore's law

 

Moore's law



“If the automobile had followed the same development cycle as the computer, a Rolls-Royce would today cost \$100, get one million miles to the gallon, and explode once a year . . .”

Robert Cringely

