

# **Digital Electronics**

## **Boolean Algebra**

Dr. Eleni Akrida  
[eleni.akrida@durham.ac.uk](mailto:eleni.akrida@durham.ac.uk)



# Overview of today's lecture


- Functionally complete sets
- Intro to Combinational Logic and Circuits
- Sum of Products vs Product of Sums
- Boolean Algebra
  - Axioms
  - Theorems

# From transistors to gates

A **NAND** gate:



A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

 

# Gates we have seen

**AND** gate:





**OR** gate:



**NOT** gate:



**NAND** gate:

  

# More Boolean operations

A	B	Y
0	0	?
0	1	?
1	0	?
1	1	?

There are  $2^{2^k}$  possible Boolean operations on  $k$  inputs –  
*i.e.* 16 on 2 inputs.

The trivial operations are: 0, 1, A, B

We have seen  $\overline{A}$ ,  $\overline{B}$ ,  $A \cdot B$ ,  $A + B$

What else is there?

Adding rule:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \text{ (with Carry)}$$

# Truth tables: Exclusive OR (XOR)

- XOR** gate:  Algebraic expression:  $Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Linear truth table

AND		B	
		0	1
A	0	0	1
	1	1	0

Rectangular/Coordinate table

# Exclusive OR (XOR)

We can construct XOR using AND, OR and NOT:

$$A \oplus B = (A + B) \cdot (\overline{A \cdot B})$$


Check:

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

# Exclusive OR (XOR)



is the same as

 



# Functionally Complete Sets

In logic, a **functionally complete set of Boolean operators** is one which can be used to *express all possible truth tables* by combining members of the set into a Boolean expression.

AND		
0	0	0
0	1	0
1	0	0
1	1	1

NOT	
0	1
1	0

OR		
0	0	0
0	1	1
1	0	1
1	1	1

XOR  
NAND  
NOR

A . B  
0 0 0  
0 0 0  
0 0 0  
0 0 0


# Functionally Complete Sets

Any logic circuit can be constructed with just these three operators

- **AND, OR, and NOT**
- They form a **functionally complete set**.

Charles Sanders Peirce (1880) showed that **NOR gates alone** form a functionally complete set.

 NOR: inverse of OR,  $Y = \overline{A + B}$



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

# NOR gates

AND:

$$A \cdot B = \overline{\overline{(A + A)} + \overline{(B + B)}}$$

OR:

$$A + B = \overline{\overline{(A + B)} + \overline{(A + B)}}$$


NOT:

$$\overline{A} = \overline{A + A}$$

$$\text{NOR } A = \text{NOR } (B \text{ NOR } B)$$

$$\begin{array}{c|c} A & A \text{ NOR } A \\ \hline 0 & 1 \\ 1 & 0 \end{array}$$

$$\begin{array}{c|c|c|c|c} A & B & \overline{A+A} & \overline{B+B} & \overline{A+B} \\ \hline 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 1 & 0 & 0 \\ 1 & 0 & 0 & 1 & 0 \\ 1 & 1 & 0 & 0 & 1 \end{array}$$

 


# Functionally Complete Sets

Any logic circuit can be constructed with just these three operators

- **AND, OR, and NOT**
- They form a **functionally complete set**.

Henry M. Sheffer (1913) showed that the **NAND gates alone** form a functionally complete set.

 NAND: inverse of AND,  $Y = \overline{A \cdot B}$



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

# NAND gates

AND:

$$A \cdot B = \overline{\overline{A \cdot B} \cdot \overline{A \cdot B}}$$


OR:

$$A + B = \overline{\overline{A \cdot A} \cdot \overline{B \cdot B}}$$

NOT:

$$\overline{A} = \overline{A \cdot A}$$

		$\alpha$	$\beta$	$\gamma$	AND	OR
A	B	$A < B$	$A < A$	$B < B$	$\alpha < \alpha$	$\beta < \beta$
0	0					
0	1					
1	0					
1	1					

 

# Digital design principles

Digital design is all about **managing the complexity** of huge numbers of interacting elements. Some principles help humans do this:

**Abstraction:** Hiding details when they aren't important.

**Discipline:** Restricting design choices to make things easier to model, design and combine. E.g. the logic families and the digital abstraction.

## The three –y's:

**Hierarchy:** dividing a system into modules and submodules

**Modularity:** well-defined functions and interfaces for modules


**Regularity:** encouraging uniformity so modules can be swapped or reused.

# Circuits

Network that processes discrete-valued variables.

A **circuit** has:

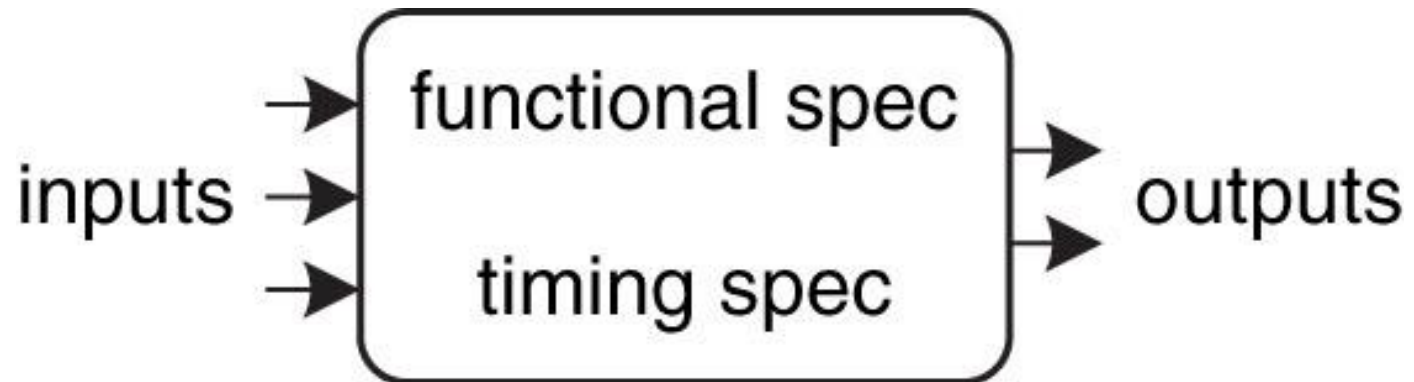
- one or more discrete valued input terminals
- one or more discrete valued output terminals
- a specification of the relationship between inputs and outputs
- a specification of the delay between inputs changing and outputs responding


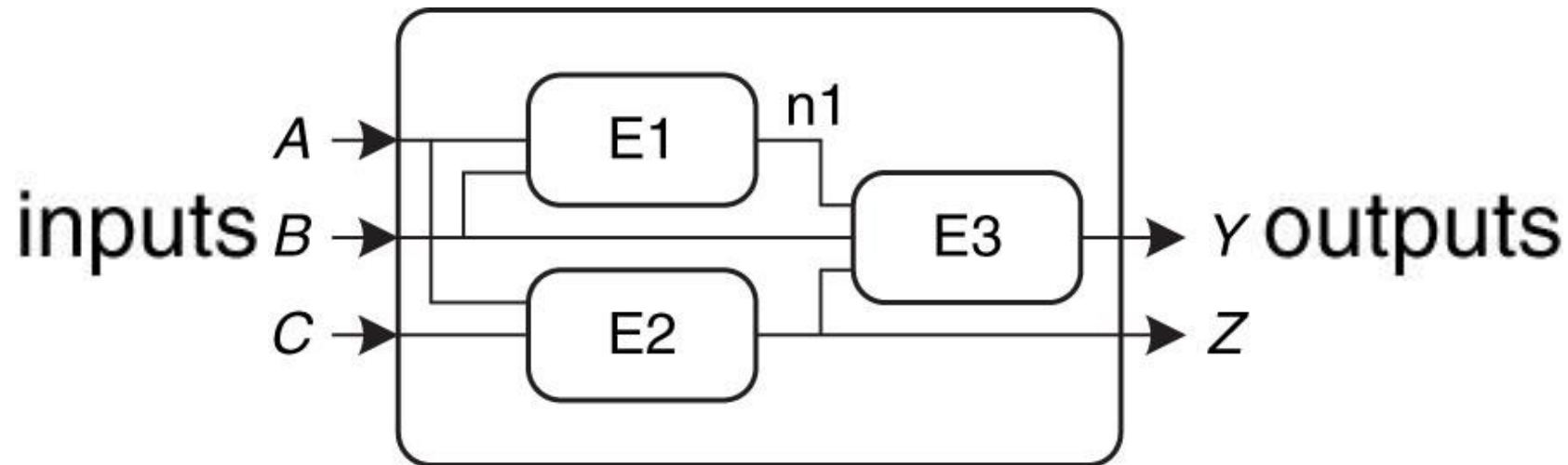
# Circuits

The circuit is made up of **elements** and **nodes**:

- An **element** is itself a circuit with inputs, outputs and specs.
- A **node** is a wire joining elements, whose voltage conveys a discrete valued variable.





# Combinational logic

We wish to design **very large** circuits to perform functions for us.







We will restrict what we allow, for now, firstly to **combinational logic\*** and circuits.

## Combinational logic rules:

- **Individual gates** are combinational circuits.
- Every circuit **element** must be a combinational circuit.
- Every node is either an **input** to the circuit or connecting **to exactly one output** of a circuit element
- The circuit has **no cyclic paths** – every path through the circuit visits any node at most once.

      
# Combinational logic

Which of these are combinational circuits and why?


 
# Boolean Algebra

- The algebra of 0/1 variables.
- Used for specifying the function of a combinational circuit
- Used to analyse and simplify the circuits required to give a specified truth table.



# Boolean Algebra

$$A \cdot A \equiv A$$

- **Variables** are represented by letters, e.g.  $A, B, C$ ...  
The **complement** or **inverse** of a variable is written with a bar, e.g.  $\bar{A}$ .

- A variable or its complement is called a **literal**, e.g.  $A, \bar{A}, B$  or  $\bar{B}$ .

- The AND of several literals is called a **product**, e.g.  $\bar{A}\bar{B}C$  or  $A\bar{C}$ ,  
Products may be written  $A \cdot B \cdot C, ABC, A \cap B \cap C$  or  $A \wedge B \wedge C$ .

A **minterm** is a product in which **all** the inputs to a function appear once each (either in its complemented or uncomplemented form).

$$\begin{array}{c} \overline{A \bar{A} \bar{B} C} = \overline{A \bar{B} C} \\ \hline \begin{array}{ccc|c} \bar{A} & A & \bar{A} & \\ 0 & 0 & 0 & \\ 1 & 1 & 1 & \end{array} \end{array}$$

$$1 \cdot 0 \cdot 0 = 0$$

- The OR of several literals is called a **sum** or **implicant**, e.g.  $A + B + C$  or  $A + C$   
Sums may be written  $A + B + C, A \cup B \cup C$  or  $A \vee B \vee C$ .

$$1 + 1 + 0 = 1 \quad 0 + 0 + 0 = 0$$

A **maxterm** is a sum in which **all** the inputs to a function appear once each (either in its complemented or uncomplemented form).

# Truth table to Boolean eqn.

X	Y	Z	F(X,Y,Z)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Total Variable = 5

$$\bar{x}(\bar{y}\bar{z} + yz)$$

$$2^5 x(\bar{y}z + y\bar{z})$$

$$\bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}z + xy\bar{z}$$

1 if any input is 1  
0

$$(x+y+\bar{z})(\bar{x}+y+\bar{z})(x+\bar{y}+\bar{z}) + (\bar{x}+\bar{y}+z)$$

POS

$$AB + AC = A(B + C)$$

# Truth table to Boolean eqn.

## “Sum of products” form

Every Boolean expression can be written as minterms **ORed together**:

$$(A \cdot B \cdot C) + (A \cdot \bar{B} \cdot \bar{C}) + (\bar{A} \cdot B \cdot C)$$

## “Product of sums” form

Also every Boolean expression can be written as maxterms **ANDed together**:

$$(\bar{A} + \bar{B} + \bar{C}) \cdot (\bar{A} + B + C) \cdot (A + B + \bar{C})$$

# Truth table to SOP

X	Y	Z	F(X,Y,Z)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Each row can be represented by a minterm that is true:

$$\bar{X} \cdot \bar{Y} \cdot \bar{Z}$$

FGPA


$$\bar{X} \cdot Y \cdot \bar{Z}$$

$$X \cdot \bar{Y} \cdot Z$$

**OR** together the **1 values** of the function, to give SOP form:

$$F(X,Y,Z) = \bar{X} \cdot \bar{Y} \cdot \bar{Z} + \bar{X} \cdot Y \cdot \bar{Z} + X \cdot \bar{Y} \cdot Z + X \cdot Y \cdot \bar{Z}$$

# Example

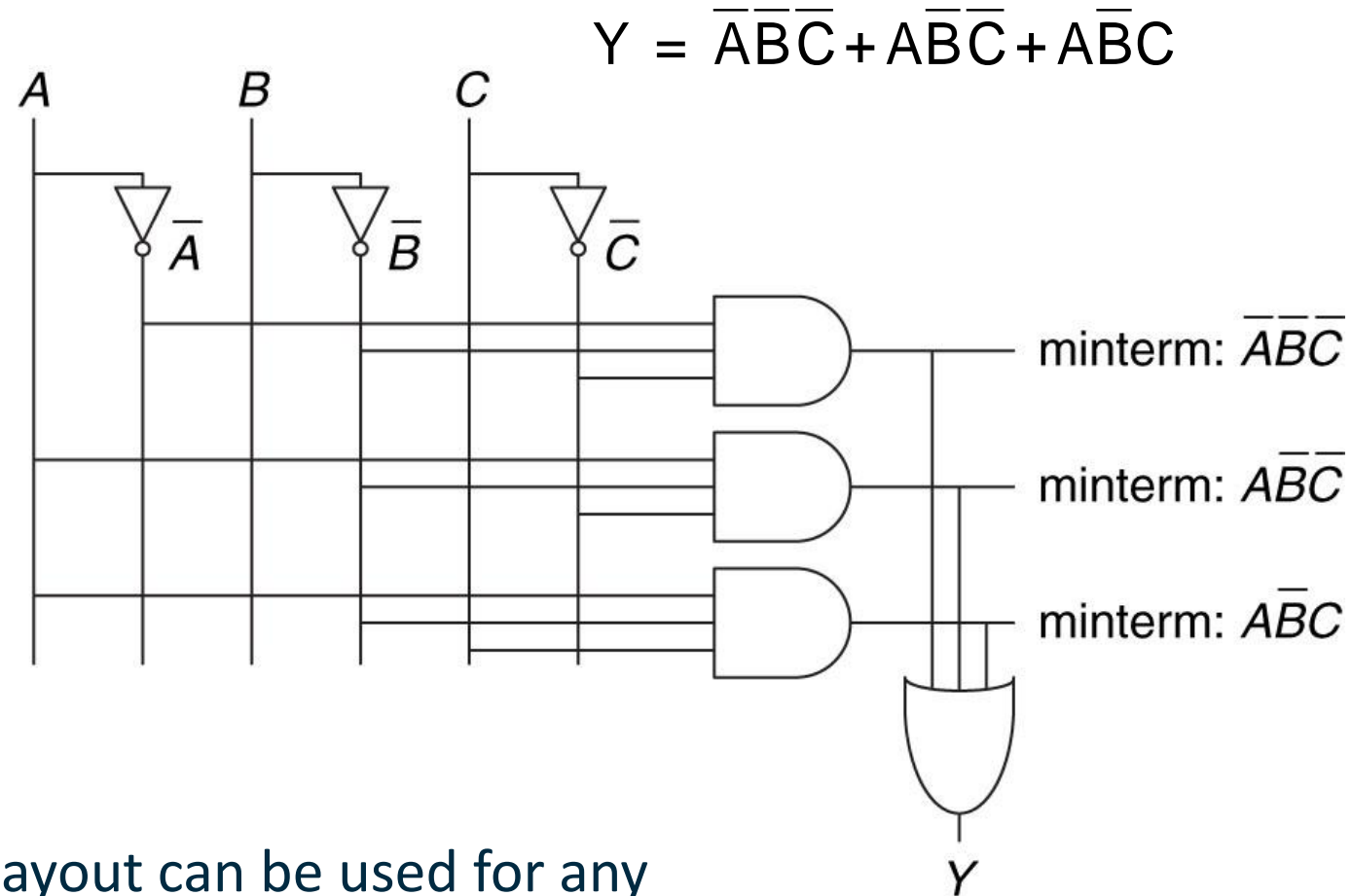

This layout can be used for any sum-of-products expression.



# Truth table to POS

X	Y	Z	F(X,Y,X)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Each row can be represented by a maxterm that is false:

$$X + Y + Z$$

$$X + \bar{Y} + Z$$

$$\bar{X} + Y + \bar{Z}$$

**AND** together the **0 values** of the function, to give POS for F:

$$F(X,Y,Z) = (X + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + Y + Z)(\bar{X} + \bar{Y} + \bar{Z})$$

Compare to  $F(X,Y,Z) = \bar{X} \cdot \bar{Y} \cdot \bar{Z} + \bar{X} \cdot Y \cdot Z + X \cdot \bar{Y} \cdot Z + X \cdot Y \cdot \bar{Z}$

# Boolean Algebra

Two equivalent expressions for the same logical formula:

$$F(X,Y,Z) = (X + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + Y + Z)(\bar{X} + \bar{Y} + \bar{Z})$$

$$F(X,Y,Z) = \bar{X} \cdot \bar{Y} \cdot \bar{Z} + \bar{X} \cdot Y \cdot Z + X \cdot \bar{Y} \cdot Z + X \cdot Y \cdot \bar{Z}$$

Which is simpler?

Is there another equivalent expression that is simpler than either?

We will use **Boolean algebra** and **Karnaugh maps** to produce the simplest equivalent expression that can then be turned into circuitry.

# Axioms of Boolean Algebra

Axiom		Dual axiom		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \cdot 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \cdot 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \cdot 1 = 1 \cdot 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Axioms cannot be proven – they are defined or assumed.  
Each axiom has a dual obtained by interchanging AND and OR,  
and 0 and 1.

# Theorems of one variable

Theorem		Dual theorem		Name
T1	$B \cdot 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \cdot 0 = 0$	T2'	$B + 1 = 1$	Null element
T3	$B \cdot B = B$	T3'	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$			Involution
T5	$B \cdot \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

Theorems can be proved by applying the axioms and checking cases

$$\begin{array}{c|c}
 B & B \cdot \overline{B} \\
 \hline
 0 & 0 \cdot 1 = 0 \\
 1 & 1 \cdot 0 = 0
 \end{array}$$

$$\begin{array}{c|c}
 B & B + \overline{B} \\
 \hline
 0 & 0 + 1 = 1 \\
 1 & 1 + 0 = 1
 \end{array}$$

# Theorems of several variables

	Theorem	Dual	Name
T6	$B \cdot C = C \cdot B$	$B + C = C + B$	Commutativity
T7	$(B \cdot C) \cdot D = B \cdot (C \cdot D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \cdot (C + D) = B \cdot C + B \cdot D$	$(B + C) \cdot (B + D) = B + (C \cdot D)$	Distributivity
T9	$B \cdot (B + C) = B$	$B + (B \cdot C) = B$	Covering
T10	$B \cdot C + B \cdot \bar{C} = B$	$(B + C) \cdot (B + \bar{C}) = B$	Combining
T11	$B \cdot C + \bar{B} \cdot D + C \cdot D = B \cdot C + \bar{B} \cdot D$		Consensus
T11'	$(B + C) \cdot (\bar{B} + D) \cdot (C + D) = (B + C) \cdot (\bar{B} + D)$		
T12	$\overline{B_0 \cdot B_1 \cdot B_2 \dots} = \bar{B}_0 + \bar{B}_1 + \bar{B}_2 \dots$		De Morgan's
T12'	$\overline{\bar{B}_0 + \bar{B}_1 + \bar{B}_2 \dots} = \bar{B}_0 \cdot \bar{B}_1 \cdot \bar{B}_2 \dots$		

$$B \cdot (B + C)$$

$$B \cdot B + B \cdot C$$

$$B + B \cdot C$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A \cdot B \cdot C \cdot D} = \bar{A} + \bar{B} + \bar{C} + \bar{D}$$

# Theorems of several variables

Theorem	Dual	Name
<p><b>Key principle for simplification:</b></p> <p>use T10 and T11 to remove variables or terms</p> <p>use others to rearrange so that T10 or T11 can be applied</p>		
T10	$B \cdot C + B \cdot \bar{C} = B$ $(B + C) \cdot (B + \bar{C}) = B$	Combining
T11	$B \cdot C + \bar{B} \cdot D + C \cdot D = B \cdot C + \bar{B} \cdot D$	Consensus
T11'	$(B + C) \cdot (\bar{B} + D) \cdot (C + D) = (B + C) \cdot (\bar{B} + D)$	
<p>General form of T10: for any implicant (i.e., product or sum) P and variable A,</p> $PA + P\bar{A} = P$ <p><i><math>P(A + \bar{A}) = P \cdot 1 = P</math></i></p>		

# DeMorgan's Theorem

Proof of two variable case:

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

Proof:

$A$	$B$	$A \cdot B$	$\overline{A \cdot B}$	$\overline{A}$	$\overline{B}$	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

# Example

Write out the sum of products form

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Sum of products:  $Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C}$

Now minimise this equation.

$$Y = (\bar{A} + A)\bar{B}\bar{C} + A\bar{B}C$$

$$Y = (1)\bar{B}\bar{C} + A\bar{B}C$$

$$Y = \bar{B}\bar{C} + A\bar{B}C$$

Handwritten derivation:

$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} = \bar{B}\bar{C}(\bar{A} + A) = \bar{B}\bar{C}$$



# Example

Write out the sum of products form

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Sum of products:  $Y = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C$


$$\overline{A}\overline{B}C = \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C}$$

Now minimise this equation.

$$Y = (\overline{A} + A)\overline{B}\overline{C} + A\overline{B}(C + \overline{C})$$


$$Y = \overline{B}\overline{C} + A\overline{B}$$

# Example

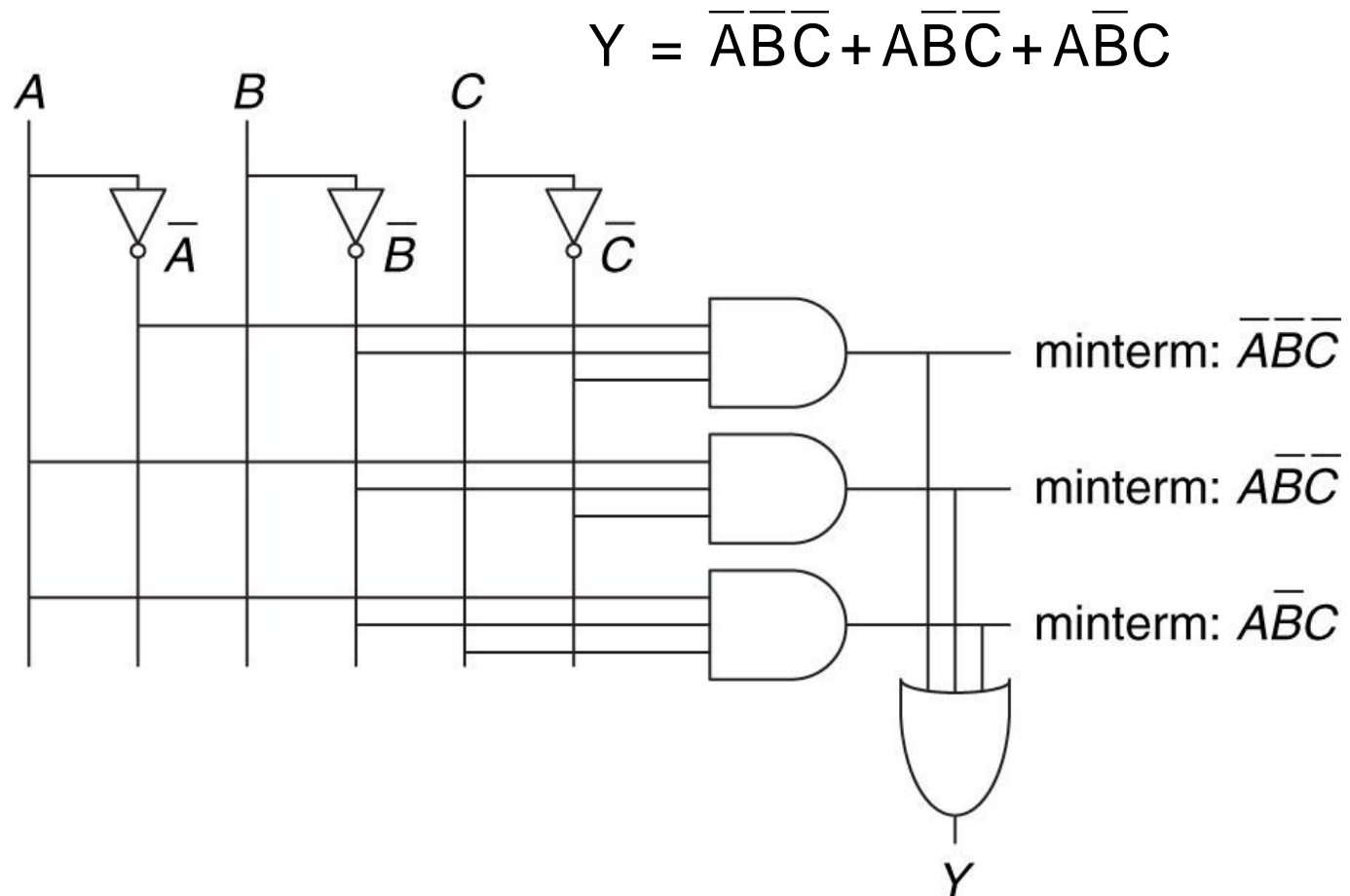
 
# Example

$$Y = \overline{B}\overline{C} + A\overline{B}$$



The simplified expression gives the same logical output with much less hardware.